


# NDA-CDS 2 2024

# GS

LIVE

# PHYSICS

CLASS 10

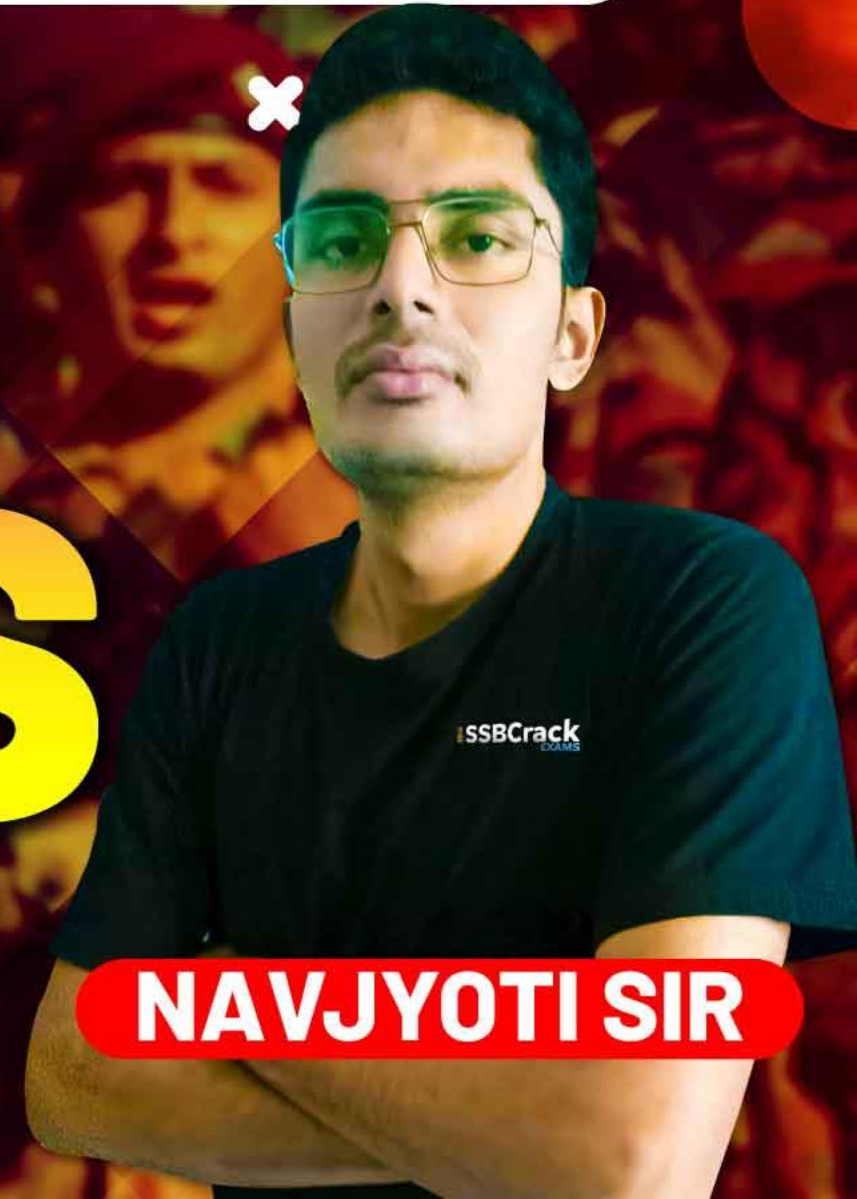

NAVJYOTI SIR



## 11 July 2024 Live Classes Schedule

8:00AM	11 JULY 2024 DAILY CURRENT AFFAIRS	RUBY MA'AM
9:00AM	11 JULY 2024 DAILY DEFENCE UPDATES	DIVYANSHU SIR

### SSB INTERVIEW LIVE CLASSES

9:00AM	OVERVIEW OF GPE & PRACTICE SESSION	ANURADHA MA'AM
--------	------------------------------------	----------------

### NDA 2 2024 LIVE CLASSES

1:00PM	GS - PHYSICS - CLASS 10	NAVJYOTI SIR
4:00PM	MATHS - BINARY NUMBERS	NAVJYOTI SIR
5:30PM	ENGLISH - SENTENCE COMPLETION - CLASS 1	ANURADHA MA'AM

### CDS 2 2024 LIVE CLASSES

1:00PM	GS - PHYSICS - CLASS 10	NAVJYOTI SIR
5:30PM	ENGLISH - SENTENCE COMPLETION - CLASS 1	ANURADHA MA'AM



# **ELECTRICITY**

---



# WHAT WILL WE STUDY ?

- Charges and Static Electricity
- Coulomb's Law of Electrostatics
- Electric Field
- Electric Potential and Potential Difference
- Electric Current
- Ohm's Law
- Resistance and Resistivity
- Combination of Resistors
- Internal Resistance, Series and Parallel Combination of Cells
- Kirchoff's Law
- Electric Energy, Power and Heating Effects



# **CHARGE**

- **Charge is that property of an object by virtue of which it apply electrostatic force of interaction on other objects.**
- **Charges are of two types (i) Positive charge (ii) Negative charge**
- **Like charges repel and unlike charges attract each other.**



# BASIC PROPERTIES OF CHARGE

## Additivity of Charge

If a system consists of  $n$  charges  $q_1, q_2, q_3, \dots, q_n$ , then the total charge of the system will be  $q_1 + q_2 + q_3 + q_4 + \dots + q_n$ .

- Quantisation of Charge : Charge on any object can be an integer multiple of a smallest charge ( $e$ ).

*charge on an electron,*



$$Q = \pm ne$$

where,  $n = 1, 2, 3, \dots$  and  $e = 1.6 \times 10^{-19} \text{ C}$ .

*SI unit of charge = Coulomb.*

- Conservation of Charge : Charge can neither be created nor be destroyed, but can be transferred from one object to another object.

# STATIC ELECTRICITY

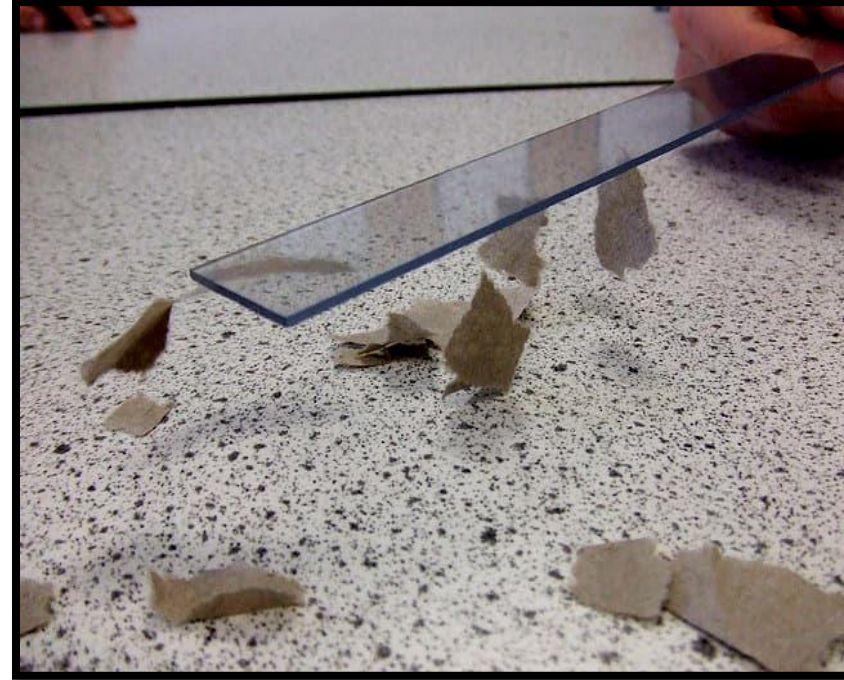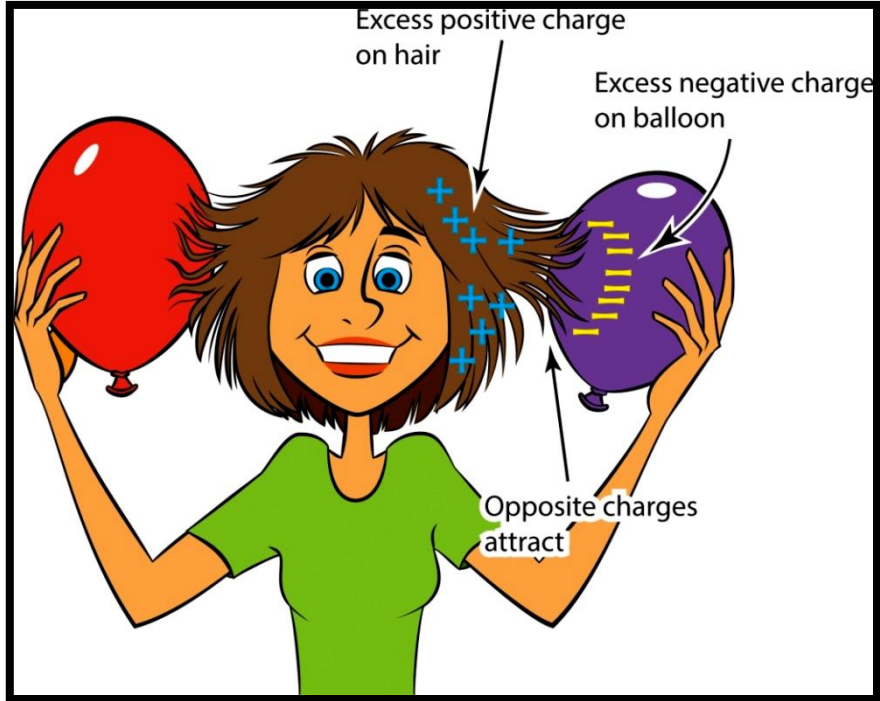

*charges are not moving,*

# Coulomb's Law

- The force of interaction between any two point charges is directly proportional to the product of the charges and inversely proportional to the square of the distance between them.

Suppose two point charges  $q_1$  and  $q_2$  are separated in vacuum by a distance  $r$ , then force between two charges is given by

$$F_e = \frac{K|q_1q_2|}{r^2}$$

$F_e$  can be attractive & repulsive,

$F_e < 0$  — attractive,  $F_e > 0$  — repulsive,



forces of equal magnitude,

$$-\frac{kq_1q_2}{r^2}$$




# Electric Field

- The space in the surrounding of any charge in which its influence can be experienced by other charges.

$$\text{Electric field intensity } \mathbf{E} = \lim_{q_0 \rightarrow 0} \frac{\mathbf{F}}{q_0}$$

*Lines of electric field*

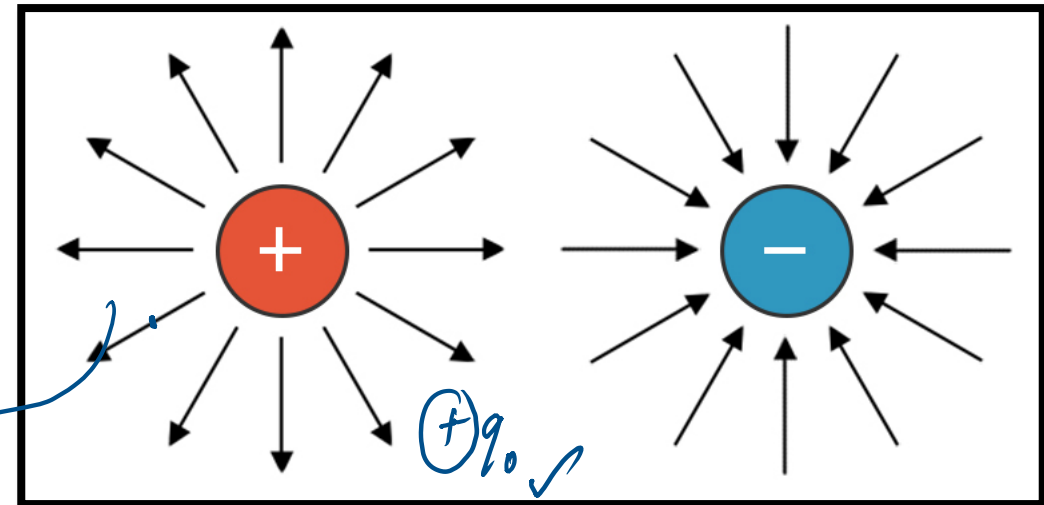

- It is a vector quantity and its direction is in the direction of electrostatic force acting on positive charge.
- Its SI unit is NC<sup>-1</sup> or V/m.

# ELECTRIC POTENTIAL


- Electric potential at any point is equal to the work done per unit positive charge in carrying it from infinity to that point in electric field.

$$V = \frac{W}{q}$$

- It is a scalar quantity. Its SI unit is J/C or volt.
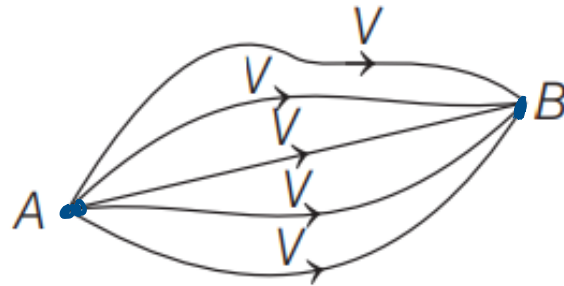
# POTENTIAL DIFFERENCE / Voltage

- The potential difference between two points A and B is equal to the work done by the external force in moving a unit positive charge against the electrostatic force from point B to A along any path between these two points.




$$\Delta V = \frac{W_{AB}}{q}$$
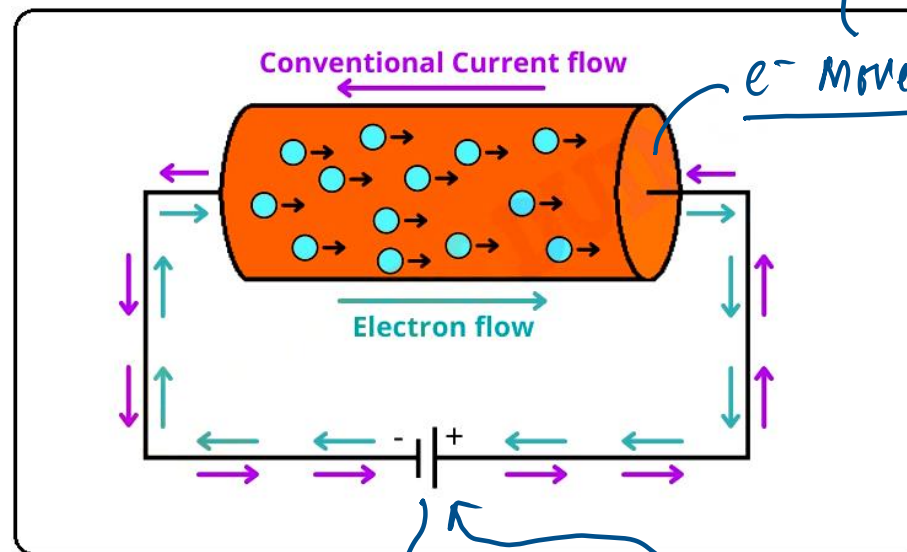
# ELECTRIC CURRENT

- Electric current  $(I) = \frac{q}{t}$ . Its SI unit is ampere (A).

- The conventional direction of electric current is opposite to the direction of motion of electrons.



drifting of  $e^-$   
drift velocity  
( $v_d$ )

$e^-$  move towards +ve terminal of battery  
(because of electric field creation)

potential difference / voltage


# DRIFT VELOCITY

When a potential difference is applied across the ends of a conductor, the free electrons in it move with an average velocity opposite to the direction of electric field, which is called drift velocity of free electrons.


$$v_d = \frac{eE\tau}{m} = \frac{eV\tau}{ml}$$

$$E = \frac{V}{L}$$

avg. relaxation time

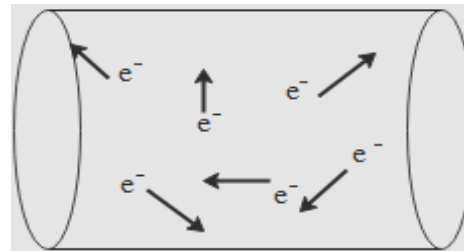

When no potential difference is applied

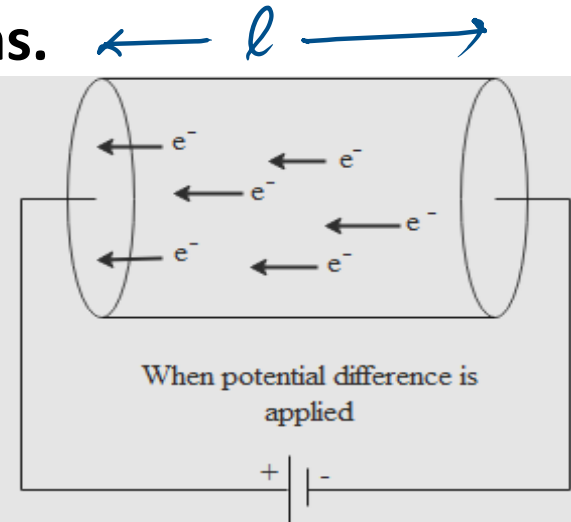

When potential difference is applied

Relation between electric current and drift velocity is given by

$$v_d = \frac{I}{An e} \quad / \quad I = neAv_d$$

$n$  - no. of e⁻ per unit vol. of conductor

$A$  - Area of cross section of conductor

avg. time of collision of e⁻,



# (#) OHM'S LAW

- If physical conditions of a conductor such as temperature remains unchanged, then the electric current (I) flowing through the conductor is directly proportional to the potential difference (V) applied across its ends.

$$\underline{I \propto V} \text{ or } V = IR$$

where,  $R$  is the electrical resistance of the conductor and

$$R = \frac{ml}{Ane^2\tau}$$

$$I = \frac{1}{R} (V) \Rightarrow \underline{V = IR}$$


$$v_d = \frac{eV\tau}{mL} \Rightarrow \underline{V = \frac{v_d mL}{e\tau}} \quad , \quad \underline{I = neAv_d}$$

# OHMIC AND NON-OHMIC RESISTANCES
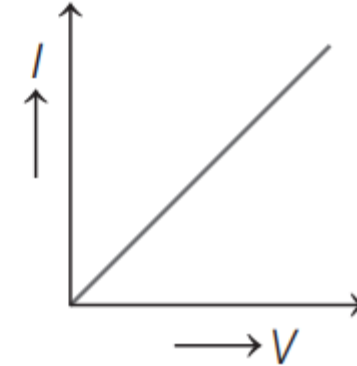
## Ohmic Conductors

Those conductors which obey Ohm's law, are called ohmic conductors, e.g. all metallic conductors are ohmic conductor.


For ohmic conductors  $V$ - $I$  graph is a straight line.


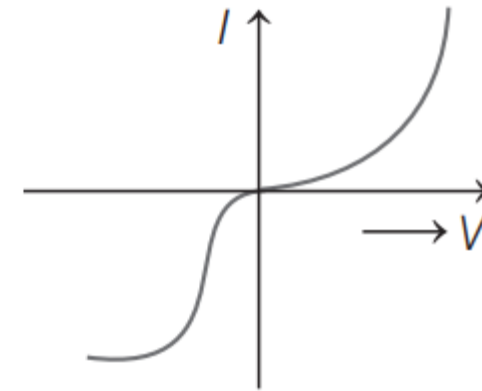
## Non-ohmic Conductors

Those conductors which do not obey Ohm's law, are called non-ohmic conductors, e.g. diode valve, triode valve, transistor, vacuum tubes etc.

For non-ohmic conductors  $V$ - $I$  graph is not a straight line.



# (examples)

# RESISTANCE

- The obstruction offered by any conductor in the path of flow of current is called its electrical resistance.

Electrical resistance of a conductor,  $R = \frac{\rho l}{A}$   
where,  $l$  = length of the conductor,  $A$  = cross-section area  
and  $\rho$  = resistivity of the material of the conductor.

SI unit  $\rightarrow$  Volt  $A^{-1}$

or ohms  
 $(\underline{\Omega})$

$$R = \frac{ml}{ne^2AT} = \rho \frac{l}{A} \quad \text{where, } \rho \rightarrow \text{resistivity}$$
$$\rho = \left( \frac{m}{ne^2T} \right)$$

of material,  
Factors

- ①  $R \propto l$  - length of conductor
- ②  $R \propto \frac{1}{A}$  - area of cross section

# RESISTIVITY


Resistivity of a material of a conductor is given by

$$\rho = \frac{m}{ne^2\tau}$$

where,  $n$  = number of free electrons per unit volume.


Resistivity is low for metals, more for semiconductors and very high for alloys like nichrome, constantan etc.

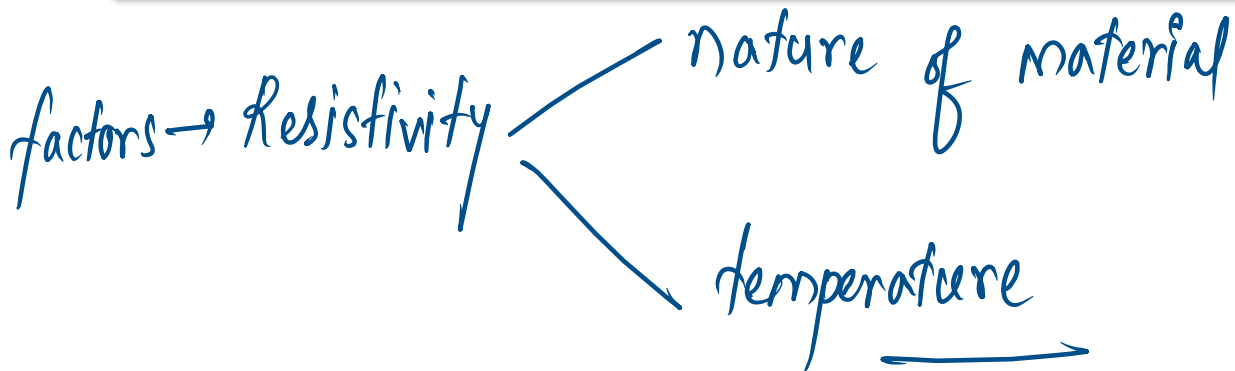Resistivity of a material depend on temperature and nature of the material. It is independent of dimensions of the conductor, i.e. length, area of cross-section etc.



# COMBINATION OF RESISTORS

## Series Circuit

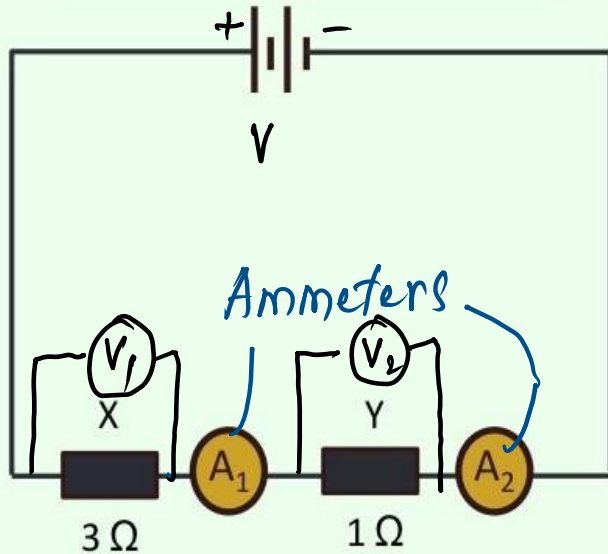


Current has only one path to flow ✓

Reading on A1 = Reading on A2

Same current flows through each resistor

$$V = V_1 + V_2$$

## Parallel Circuit

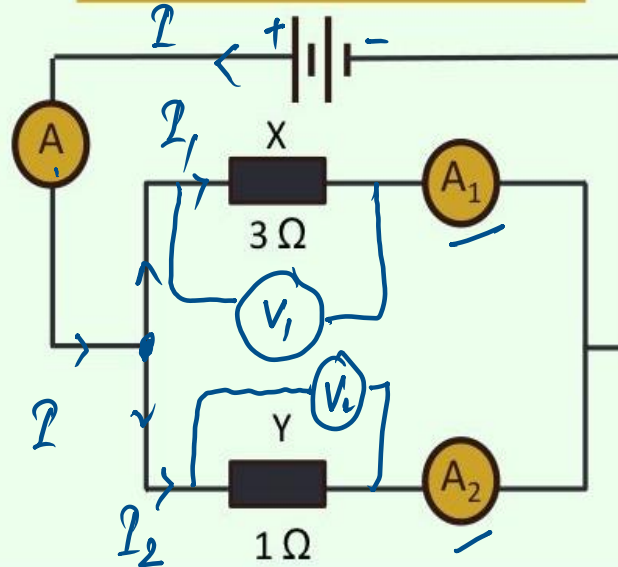

Current splits into different paths

Reading on A = Reading on A1 + A2

Main current is shared between the two resistors


$A_1, A_2$  — device to measure current

$$V_1 = V_2$$

$$I = I_1 + I_2$$




# COMBINATION OF RESISTORS

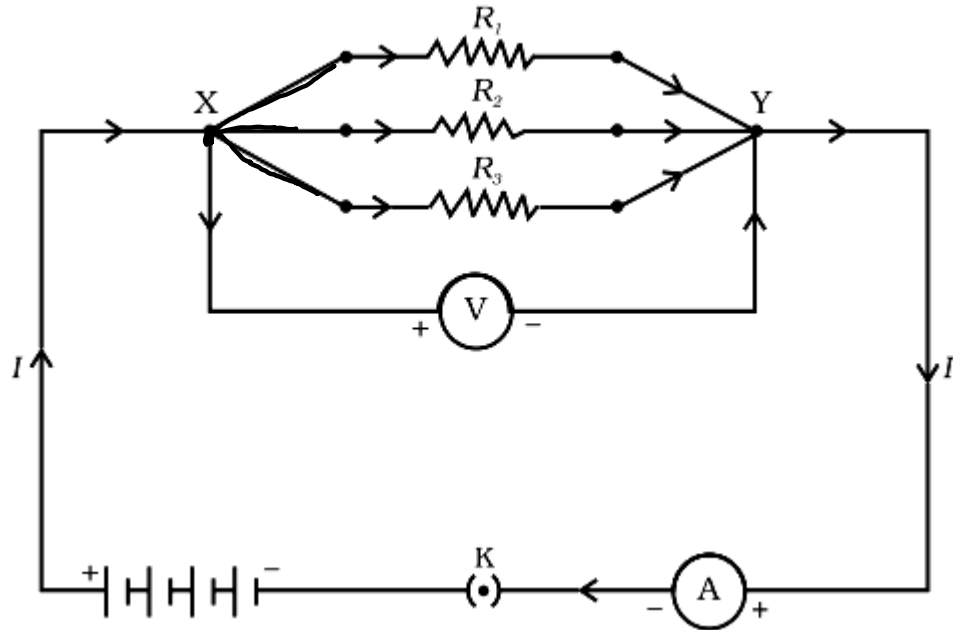

(parallel connection)

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

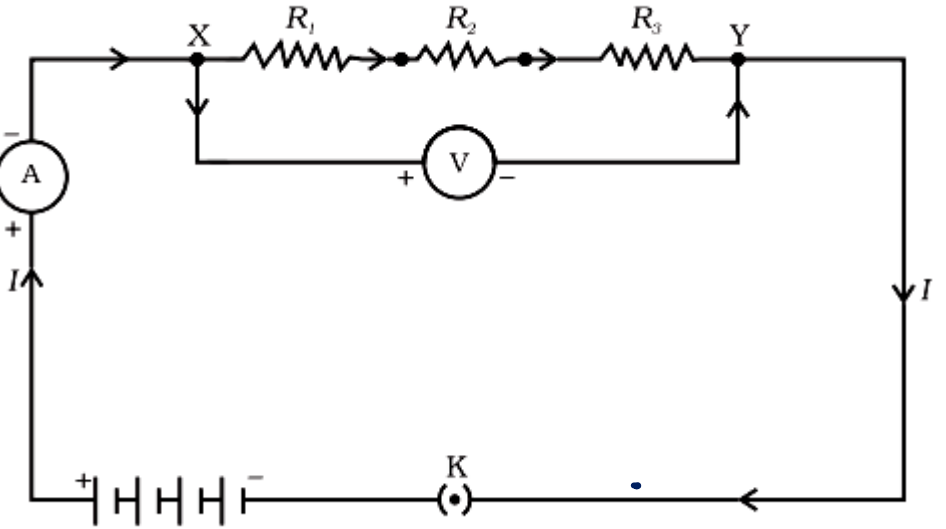for 2 resistors,  $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_2 + R_1}{R_1 R_2} \Rightarrow$




(series)

$$R = R_1 + R_2 + R_3$$

$$R = \frac{R_1 R_2}{R_1 + R_2}$$

for  $n$  equal resistances  $R \Omega$ ,

Total resistance,

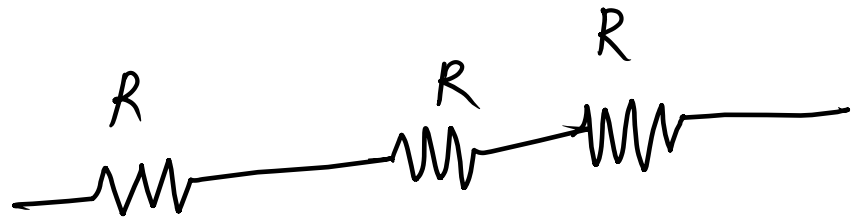

→ SERIES : Total resistance =  $R + R + R \dots n$  times

$$(R_t) \quad R_t = nR$$

→ PARALLEL : Total resistance  $\Rightarrow \frac{1}{R_t} = \frac{1}{R} + \frac{1}{R} + \dots + \frac{1}{R}$

$(R_t)$

$$\frac{1}{R_t}$$

$$= \frac{n}{R}$$

$\Rightarrow$

$$R_t = \frac{R}{n}$$

# CELLS AND INTERNAL RESISTANCE




$\mathcal{E}$  — emf

$$V = \mathcal{E} - Ir$$

$V$  — voltage


# CELLS – SERIES AND PARALLEL CONNECTION

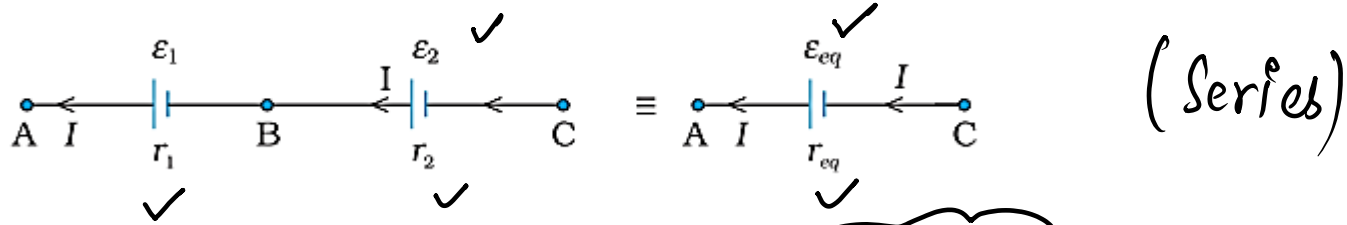

$$\epsilon_{eq} = \epsilon_1 + \epsilon_2$$
$$r_{eq} = r_1 + r_2$$

$$I = \frac{\epsilon_{eq}}{r_{eq}}$$

# CELLS – SERIES AND PARALLEL CONNECTION

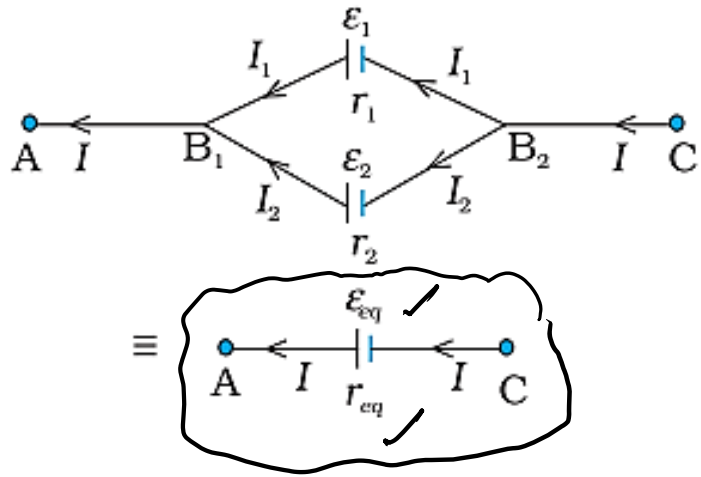

$$\frac{1}{r_{eq}} = \frac{1}{r_1} + \dots + \frac{1}{r_n}$$

$$\frac{\mathcal{E}_{eq}}{r_{eq}} = \frac{\mathcal{E}_1}{r_1} + \dots + \frac{\mathcal{E}_n}{r_n} \quad \Rightarrow \quad \underline{\underline{\mathcal{E}_{eq}}} = \left( \frac{\mathcal{E}_1}{r_1} + \dots \right) r_{eq}$$

For 2 cells,

Total  
emf, —

$$\underline{\underline{\mathcal{E}}} = \frac{\mathcal{E}_1}{r_1} + \frac{\mathcal{E}_2}{r_2} \quad \Bigg/ \quad \frac{1}{r_1} + \frac{1}{r_2}$$



# KIRCHOFF'S LAWS

(i) **Junction Rule** The algebraic sum of all currents meeting at a junction in a closed circuit is zero, *i.e.*  $\Sigma I = 0$ .


This law follows law of conservation of charge.

$(\text{sum of currents})_{in} = (\text{sum of currents})_{out}$

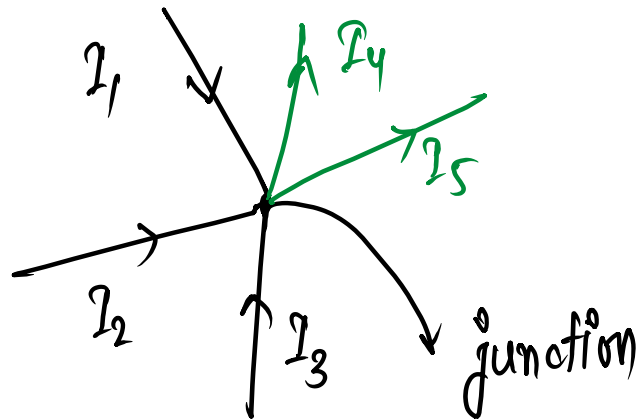(ii) **Loop Rule** The algebraic sum of all the potential differences in any closed circuit is zero, *i.e.*

$$\Sigma \Delta V = 0$$

This law follows law of conservation of energy.



$$I_1 + I_2 + I_3 - I_4 - I_5 = 0$$

$$I_1 + I_2 + I_3 = I_4 + I_5$$

# ELECTRIC ENERGY

The energy supplied by any source in maintaining the current in the electric circuit is called electric energy consumed by the electric circuit.

$$\text{Electric energy } (W) = Vq = \underbrace{VI}_{\downarrow} \underbrace{t}_{\downarrow} = \underbrace{I^2 R}_{\downarrow} \underbrace{t}_{\downarrow} = \frac{V^2}{R} t$$

Its SI unit is joule (J) but another unit is watt-hour. The bigger unit of electric energy is kilowatt hour (kWh). It is known as Board of Trade (BOT) unit.

$$\begin{aligned} 1 \text{ kilowatt hour} &= 1000 \text{ watt} \times 1 \text{ hour} \\ &= 1000 \text{ J/s} \times 3600 \text{ s} \checkmark \\ &= 3.6 \times 10^6 \text{ J} \end{aligned}$$

$$V = \frac{W}{q}$$

$$\underline{W} = \underline{Vq}$$

work done as  
electrical energy,

$$W = V(I \times t)$$

$$E = VIt$$

# ELECTRIC POWER

The electrical energy produced or consumed per unit time is called electric power.

$$\text{Electric power, } P = VI = I^2R = \frac{V^2}{R}$$

where,  $V$  is the potential difference across the conductor,  $I$  is current flowing through the conductor and  $R$  is the resistance.

Its SI unit is watt (W).

$$E = VIt$$

$$\text{Power} = \frac{E}{t} = \boxed{VI}$$

$$\boxed{VI}$$

$$V\left(\frac{V}{R}\right) = \frac{V^2}{R} \quad (\text{parallel connection})$$

$$(IR)I = I^2R \quad (\text{series connection})$$

# HEATING EFFECT

- When current  $I$  flows through a conductor of resistance  $R$  for a time  $t$ , then heat generated in it is given by ,

$$H = I^2 R t$$

Joule's law of heating,

$$H \propto I^2$$

$$H \propto R$$

$$H \propto t \text{ (current flow time — appliance is switched on time)}$$

# SUMMARY

- **Charges and Static Electricity**
- **Coulomb's Law of Electrostatics**
- **Electric Field**
- **Electric Potential and Potential Difference**
- **Electric Current**
- **Ohm's Law**
- **Resistance and Resistivity**
- **Combination of Resistors**
- **Kirchoff's Law**
- **Electric Energy and Heating Effects**





Which one of the following is primarily responsible for conduction of current in a metal ?

- (a) Bound electrons
- (b) Free electrons
- (c) Both bound and free electrons
- (d) Ions


Which one of the following is primarily responsible for conduction of current in a metal ?

- (a) Bound electrons
- (b) Free electrons
- (c) Both bound and free electrons
- (d) Ions

**ANS : B**
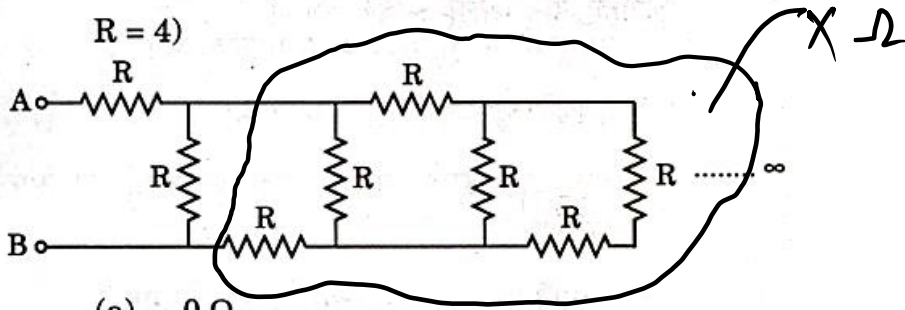
# NDA & CDS 2 2024 PHYSICS - CLASS 11

An infinite combination of resistors, having resistance  $R = 4 \Omega$ , is given below. What is the net resistance between the points A and B? (Each resistance is of equal value,  $R = 4$ )





- (a)  $0 \Omega$
- ✓ (b)  $2 + 2\sqrt{5} \Omega$
- (c)  $2 + \sqrt{5} \Omega$
- (d)  $\infty \Omega$

$$X = \left( \frac{4X}{4+X} \right) + 4$$

$R'$

$$4X + X^2 = 4X + 16 + 4X$$

$$\underline{X^2 - 4X - 16 = 0}$$

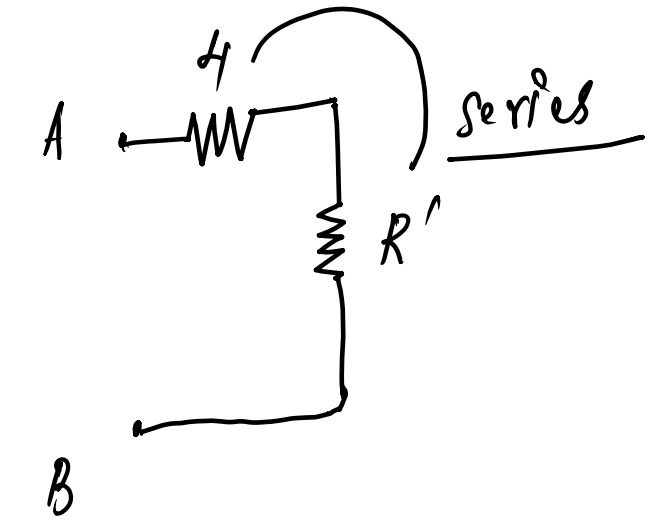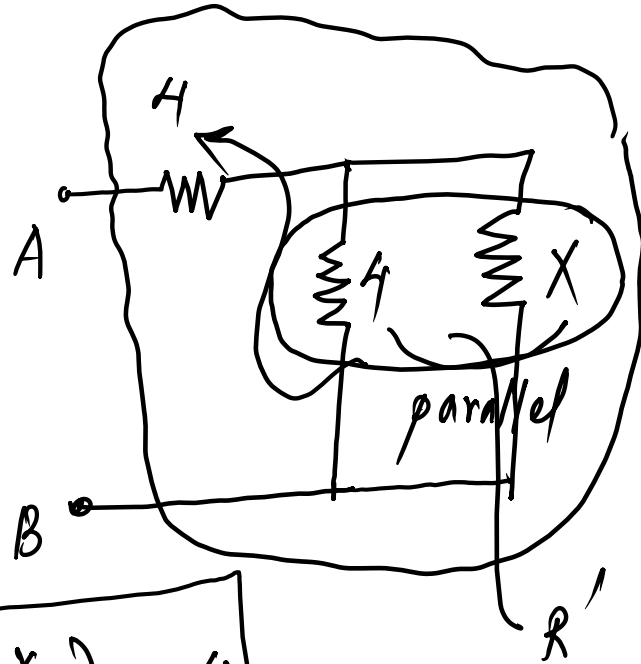


$$X = \frac{4 \pm \sqrt{16 + 64}}{2}$$

$$X = \frac{4 \pm \sqrt{80}}{2} = \frac{4 \pm 4\sqrt{5}}{2}$$

$2 + 2\sqrt{5}$   
 (-ve - not possible)  
 $2 - 2\sqrt{5}$
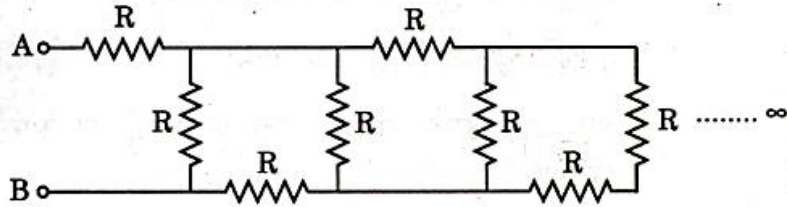
## NDA & CDS 2 2024 PHYSICS - CLASS 11

An infinite combination of resistors, having resistance  $R = 4 \Omega$ , is given below. What is the net resistance between the points A and B? (Each resistance is of equal value,  $R = 4$ )




- (a)  $0 \Omega$
- (b)  $2 + 2\sqrt{5} \Omega$
- (c)  $2 + \sqrt{5} \Omega$
- (d)  $\infty \Omega$

**Answer: (B)**

NDA & CDS 2 2024 PHYSICS - CLASS 11

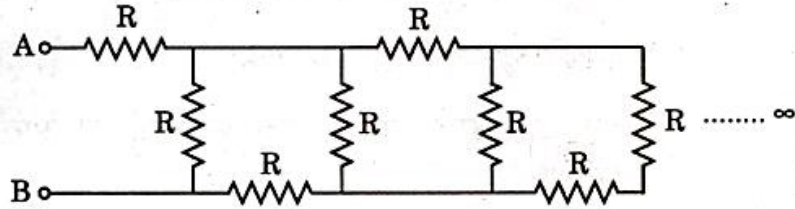
51. An infinite combination of resistors, each having resistance  $R = 4 \Omega$ , is given below. What is the net resistance between the points A and B? (Each resistance is of equal value,  $R = 4$ )



- (a)  $0 \Omega$
- (b)  $2 + 2\sqrt{5} \Omega$
- (c)  $2 + \sqrt{5} \Omega$
- (d)  $\infty \Omega$
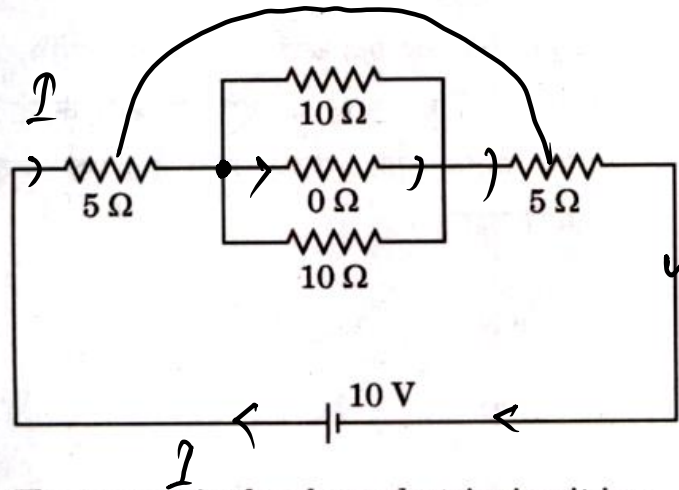
## NDA & CDS 2 2024 PHYSICS - CLASS 11

Consider the following electric circuit :



The current in the above electric circuit is :

- ✓ (a) 1 A
- (b) (10/15) A
- (c) 2 A
- (d) 1.5 A

current will always go through least resistive  
path.

So, path is having only  $5\Omega$  and  $5\Omega$  in series,


$$R = 5 + 5 = 10 \Omega$$

$$I = \frac{V}{R} = \frac{10V}{10\Omega} = 1A$$

## NDA & CDS 2 2024 PHYSICS - CLASS 11

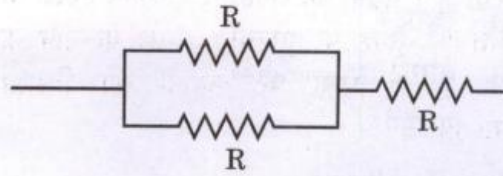1.

What is the total resistance in the following circuit element ?



(a)  $R/2$

(b)  $3R$


(c)  $3R/2$

(d)  $2R/3$


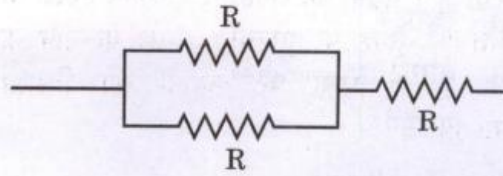
## NDA & CDS 2 2024 PHYSICS - CLASS 11

What is the total resistance in the following circuit element ?



- (a)  $R/2$
- (b)  $3R$
- (c)  $3R/2$
- (d)  $2R/3$

**Answer: (C)**

## NDA & CDS 2 2024 PHYSICS - CLASS 11

The cost of energy to operate an industrial refrigerator that consumes 5 kW power working 10 hours per day for 30 days will be  
(Given that the charge per kW.h of energy = ₹ 4)

- (a) ₹ 600
- (b) ₹ 6,000
- (c) ₹ 1,200
- (d) ₹ 1,500

## NDA & CDS 2 2024 PHYSICS - CLASS 11


The cost of energy to operate an industrial refrigerator that consumes 5 kW power working 10 hours per day for 30 days will be  
(Given that the charge per kW.h of energy = ₹ 4)

- (a) ₹ 600
- (b) ₹ 6,000
- (c) ₹ 1,200
- (d) ₹ 1,500

**Answer: (B)**
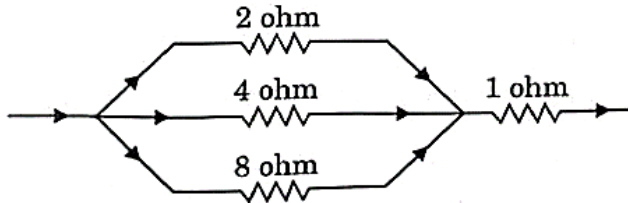
## NDA & CDS 2 2024 PHYSICS - CLASS 11

Consider the following part of an electric circuit :




The total electrical resistance in the given part of the electric circuit is

- (a)  $\frac{15}{8}$  ohm
- (b)  $\frac{15}{7}$  ohm
- (c) 15 ohm
- (d)  $\frac{17}{3}$  ohm
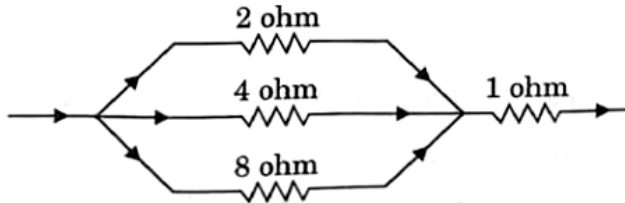
## NDA & CDS 2 2024 PHYSICS - CLASS 11

Consider the following part of an electric circuit :




The total electrical resistance in the given part of the electric circuit is

- (a)  $\frac{15}{8}$  ohm
- (b)  $\frac{15}{7}$  ohm
- (c) 15 ohm
- (d)  $\frac{17}{3}$  ohm

**Answer: (B)**

## NDA & CDS 2 2024 PHYSICS - CLASS 11

Consider the following circuit :

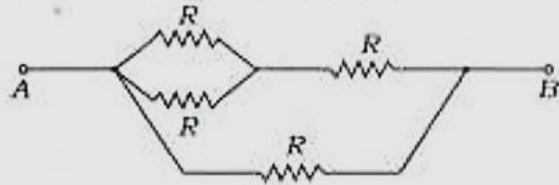


Which one of the following is the value of the resistance between points A and B in the circuit given above?

- (a)  $\frac{2}{5}R$
- (b)  $\frac{3}{5}R$
- (c)  $\frac{3}{2}R$
- (d)  $4R$

## NDA & CDS 2 2024 PHYSICS - CLASS 11

Consider the following circuit :

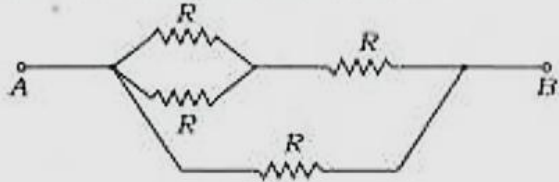

Which one of the following is the value of the resistance between points A and B in the circuit given above?

- (a)  $\frac{2}{5}R$
- (b)  $\frac{3}{5}R$
- (c)  $\frac{3}{2}R$
- (d)  $4R$

Answer: (B)

## NDA & CDS 1 2024 LIVE CLASS - PHYSICS

Which one of the following is the value of 1 kWh of energy converted into joules ?

- (a)  $1.8 \times 10^6 \text{ J}$
- (b)  $3.6 \times 10^6 \text{ J}$
- (c)  $6.0 \times 10^6 \text{ J}$
- (d)  $7.2 \times 10^6 \text{ J}$



## NDA & CDS 1 2024 LIVE CLASS - PHYSICS

Which one of the following is the value of 1 kWh of energy converted into joules ?

- (a)  $1.8 \times 10^6 \text{ J}$
- (b)  $3.6 \times 10^6 \text{ J}$
- (c)  $6.0 \times 10^6 \text{ J}$
- (d)  $7.2 \times 10^6 \text{ J}$

**Answer: (B)**

## NDA & CDS 2 2024 PHYSICS - CLASS 11

Which one of the following devices is non-ohmic ?

- (a) Conducting copper coil
- (b) Electric heating coil
- (c) Semi conductor diode
- (d) Rheostat

## NDA & CDS 2 2024 PHYSICS - CLASS 11

Which one of the following devices is non-ohmic ?

- (a) Conducting copper coil
- (b) Electric heating coil
- (c) Semi conductor diode
- (d) Rheostat

**Answer: (B)**

## NDA & CDS 2 2024 PHYSICS - CLASS 11

Which one of the following can charge an insulator ?

- (a) Current electricity
- (b) Static electricity
- (c) Magnetic field
- (d) Gravitational field

## NDA & CDS 2 2024 PHYSICS - CLASS 11

Which one of the following can charge an insulator ?

- (a) Current electricity
- (b) Static electricity
- (c) Magnetic field
- (d) Gravitational field

**Answer: (B)**

## NDA & CDS 2 2024 PHYSICS - CLASS 11

A current of  $1.0\text{ A}$  is drawn by a filament of an electric bulb for 10 minutes. The amount of electric charge that flows through the circuit is

- (a)  $0.1\text{ C}$
- (b)  $10\text{ C}$
- (c)  $600\text{ C}$
- (d)  $800\text{ C}$

## NDA & CDS 2 2024 PHYSICS - CLASS 11

A current of  $1.0\text{ A}$  is drawn by a filament of an electric bulb for 10 minutes. The amount of electric charge that flows through the circuit is

- (a)  $0.1\text{ C}$
- (b)  $10\text{ C}$
- (c)  $600\text{ C}$
- (d)  $800\text{ C}$

**Answer: (C)**

## NDA & CDS 2 2024 PHYSICS - CLASS 11

9. Which one of the following correctly represents the SI unit of resistivity?

(a)  $\Omega$

(b)  $\Omega / \text{m}$

(c)  $\Omega \text{ cm}$

(d)  $\Omega \text{ m}$



## NDA & CDS 2 2024 PHYSICS - CLASS 11

9. Which one of the following correctly represents the SI unit of resistivity?

(a)  $\Omega$

(b)  $\Omega / \text{m}$

(c)  $\Omega \text{ cm}$

(d)  $\Omega \text{ m}$

**Answer: (D)**

## NDA & CDS 2 2024 PHYSICS - CLASS 11

Which one of the following formulas does *not* represent electrical power ?

(a)  $I^2 R$

(b)  $I R^2$

(c)  $V I$

(d)  $V^2/R$

## NDA & CDS 2 2024 PHYSICS - CLASS 11

Which one of the following formulas does *not* represent electrical power ?

(a)  $I^2 R$

(b)  $I R^2$


(c)  $V I$

(d)  $V^2 / R$


**Answer: (B)**
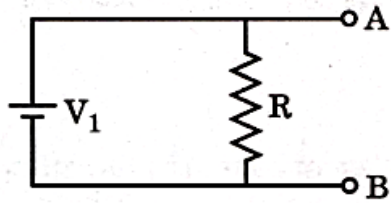
## NDA & CDS 2 2024 PHYSICS - CLASS 11

An electric circuit is given below.  $V_1 = 1\text{ V}$  and Resistance  $R = 1000\ \Omega$ .



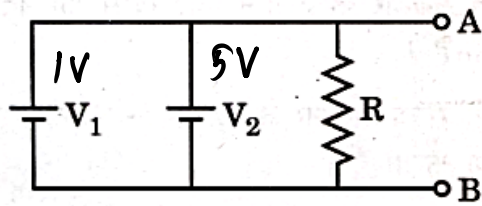The current through the resistance  $R$  is very close to  $1\text{ mA}$  and the voltage across point  $A$  and  $B$ ,  $V_{AB} = 1\text{ V}$ . Now the circuit is changed to:



where value of  $V_2 = 5\text{ V}$ . The internal resistances of both the batteries are  $0.1\ \Omega$ . The current through the resistance  $R$  is about:

- (a)  $1.0\text{ mA}$
- (b)  $1.2\text{ mA}$
- (c)  $3.0\text{ mA}$
- (d)  $5.0\text{ mA}$

as given in question,


Total voltage =  $\frac{\mathcal{E}_1}{r_1} + \frac{\mathcal{E}_2}{r_2} = \frac{1}{0.1} + \frac{5}{0.1} = \frac{6}{0.1} = 60\text{ V}$

$\frac{1}{r_1} + \frac{1}{r_2} = \frac{1}{0.1} + \frac{1}{0.1}$


$I = \frac{\text{Total voltage}}{R} = \frac{3}{1000} = 3.0 \times 10^{-3}\text{ A} = \underline{3.0\text{ mA}}$
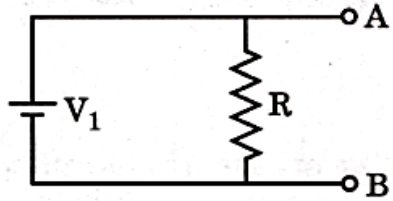
## NDA & CDS 2 2024 PHYSICS - CLASS 11

An electric circuit is given below.  $V_1 = 1\text{ V}$  and Resistance  $R = 1000\ \Omega$ .



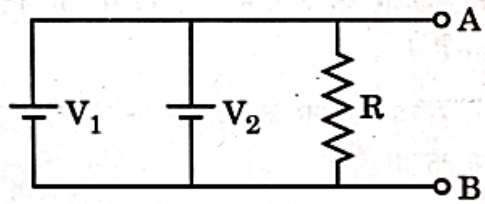The current through the resistance  $R$  is very close to  $1\text{ mA}$  and the voltage across point  $A$  and  $B$ ,  $V_{AB} = 1\text{ V}$ . Now the circuit is changed to :



where value of  $V_2 = 5\text{ V}$ . The internal resistances of both the batteries are  $0.1\ \Omega$ . The current through the resistance  $R$  is about :

- (a)  $1.0\text{ mA}$
- (b)  $1.2\text{ mA}$
- (c)  $3.0\text{ mA}$
- (d)  $5.0\text{ mA}$

**ANS : C**


# NDA-CDS 2 2024

# GS

LIVE

# PHYSICS

CLASS 11

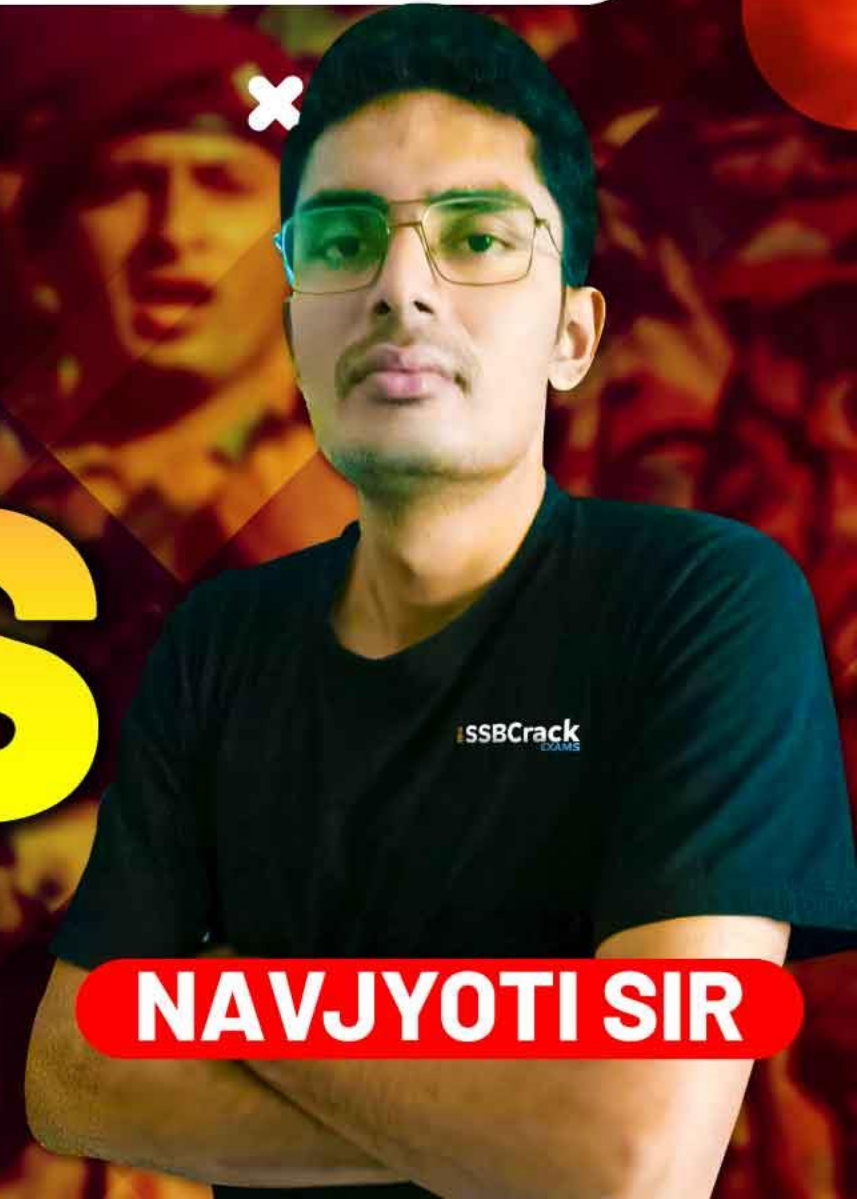

NAVJYOTI SIR